 


ECE 551

HW3

- Due Thurs March 4th in class
- Work Individually
- Remember What You Learned From the Cummings SNUG paper
- Use descriptive signal names and comment your code

HW3 Problem 1 (10pts) Trigger Logic



All trigger sources have to be high in order for **triggered** to get set.

armed is an external signal and indicates we have already sampled enough samples such that we know we can accept a trigger immediately. **triggered** cannot go high unless **armed** is asserted.

set_capture_done comes from an external control unit and is asserted once the logic analyzer has finished capturing channels into the RAMqueue. It should clear **triggered**. It should have priority over all the other signals (**armed** & the trigger sources).

Once **triggered** goes high it should stay high until **set_capture_done** knocks it down.

Reference Ex08 for what should be tested.

Submit to the dropbox: **trigger_logic.sv**, **trigger_logic_tb.sv**, and proof that you ran it.


HW3 Problem 2

You are on your own for this one. It is your SM warm up

(20pts) SM Design


A Single Slope A2D converter (capable of averaging 8 samples) was discussed in Lecture1. The block diagram is shown below. On the course webpage under HW3 you will find files:

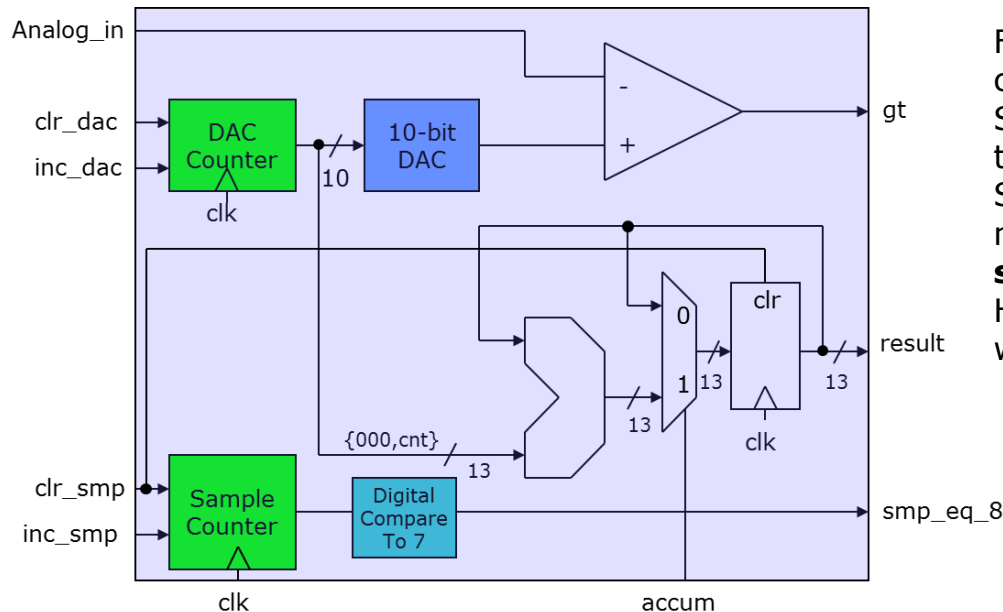ss_A2D_tb.v, ss_A2D.v, ss_A2D_datapath.v, ss_A2D_SM_shell.sv.



Flush out ss_A2D_SM_shell.sv to complete the control (state machine). Simulate your resulting design using the provided self checking test bench. Submit your verilog for the state machine (file should be called **ss_A2D_SM.sv** to the dropbox for HW3). Also submit proof that it worked.

 Hierarchy of design is as shown. Testbench instantiates DUT (ss_A2D). Which in turn instantiates datapath and statemachine. You are simply flushing out the SM code and renaming the file from ss_A2D_SM_shell.sv to ss_A2D_SM.sv. You are also simulating to prove it works.



HW3 Problem 3 (20pts) Dual PWM

Done as Exercise09 on Mon & Weds Feb 24th & Feb 26th

The project spec has a couple of slides (around slide 10) about what PWM is, and how we are using it in this project.

Create a simple 8-bit PWM block (**PWM8.sv**). Create a test bench for it and simulate/test/debug it.

Now create **dual_PWM.v** by instantiating two copies of your PWM8 block.


Submit to the dropbox:

PWM8.sv

PWM8_tb.v

dual_PWM.v


Proof that you simulated.

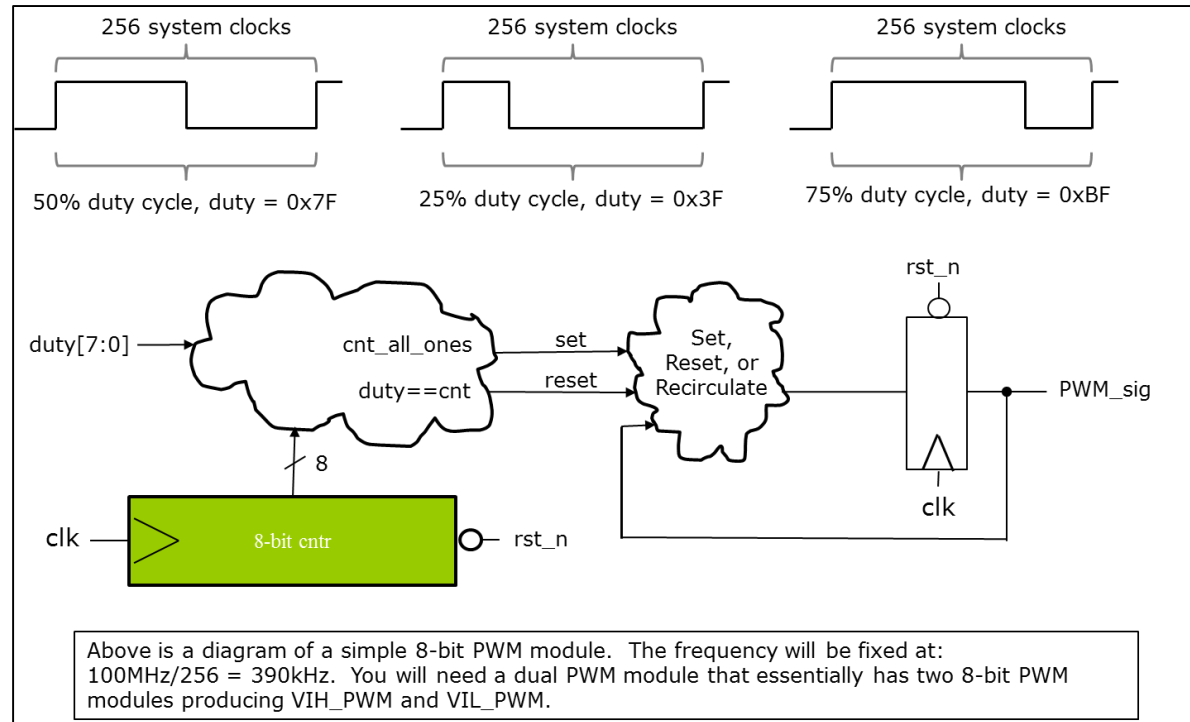

Signal:	Dir:	Description:
clk	In	100MHz main system clock
rst_n	In	Asynch active low reset
VIH[7:0],VIL[7:0]	In	8-bit vectors specifying the duty cycle (thresholds) for VIH and VIL respectively.
VIH_PWM,VIL_PWM	Out	The PWM outputs that will be low passed to create the VIL and VIH thresholds.


What is UART (RS-232)

 - RS-232 signal phases
 - Idle
 - Start bit
 - Data (8-data for our project)
 - Parity (no parity for our project)
 - Stop bit – channel returns to idle condition
 - Idle or Start next frame




- Receiver monitors for falling edge of Start bit. Counts off 1.5 bit times and starts shifting (right shifting since LSB is first) data into a register.
- Transmitter sits idle till told to transmit. Then will shift out a 9-bit (start bit appended) register at the baud rate interval.

UART Receiver/Transmitter

 

A host computer will send commands to the Logic Analyzer via a UART serial peripheral


Signal:	Dir:	Description
clk,rst_n	in	100MHz system clock & active low reset
RX	in	Serial data carrying command from host computer
rdy	out	Asserted when a byte has been received
cmd[7:0]	out	Byte received (serves as command to LA)
clr_rdy	in	Asserted to knock down the rdy signal.

 

The follower sends responses back to the host computer. These responses are sent via a UART serial peripheral.

Signal:	Dir:	Description
clk,rst_n	in	100MHz system clock & active low reset
TX	out	Serial data output back to host
trmt	in	Asserted for 1 clock to initiate transmission
tx_data[7:0]	in	Byte to transmit (response from LA)
tx_done	out	Asserted when byte is done transmitting. Stays high till next byte transmitted.

Possible Topology of UART_tx

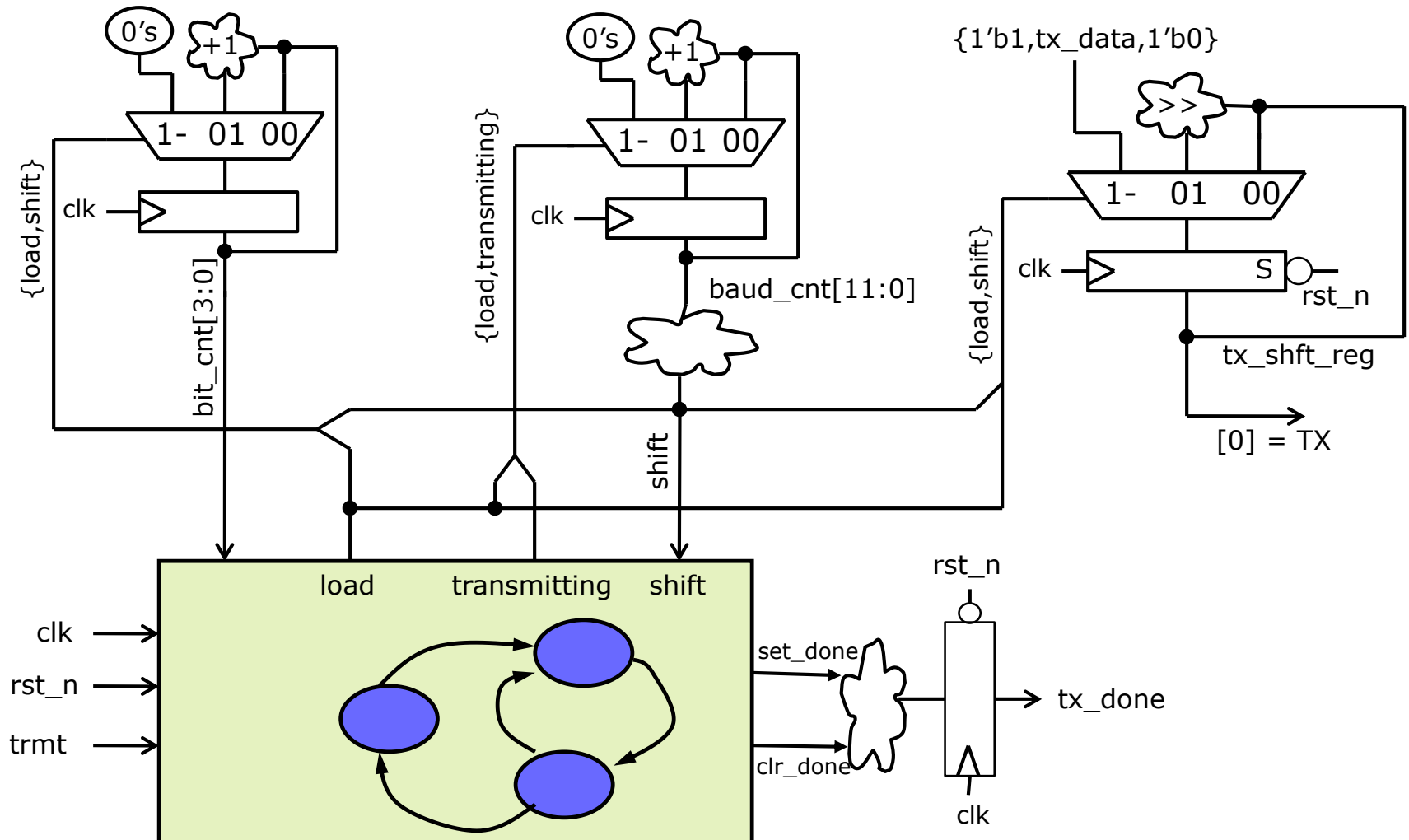

HW3 Problem 4 (20pts) UART Transmitter

Implement a the UART Transmitter (**UART_tx.sv**).

Make a simple test bench for it. This is one instance in which I would not spend too much time on the test bench. You can just instantiate your transmitter and send a few bytes. Verify the correct functionality (including baud rate) by staring at the green waveforms. You will make a more comprehensive test bench in the next problem.

Submit **UART_tx.sv** to the dropbox for HW3.

Started as Exercise10 on Fri Feb 28th

HW3 Problem 5 (20pts + 10pts) UART Receiver

Implement a the UART Receiver (**UART_rx.sv**).

Since you have a transmitter too, it is now easy to make a self checking test bench. Architect the test bench as shown. Is does the 8-bit value you transmit match the value you receive when the transmission completes.

Submit **UART_rx.sv** and your test bench to the dropbox for HW3.

