

ECE 551

HW4 *(100 pts)*

-
- Due Friday Apr 3rd @ 11:00AM
 - Work Individually
 - Use descriptive signal names
 - Comment & indent your code
 - Code will be judged on coding style

HW4 Problems 1&2 (10pts) + (10pts)

1. **(10pts)** Complete the Synopsys Design Vision tutorial. Sign below, (preferably in blood).

I, _____ completed the Synopsys Design Vision tutorial. If I had any problems with it, I discussed them with the TA or Instructor, either in person, or through email.

2. **(10pts)** Project Team Formation....become one with yourself:

I, _____ am a team of 1 and I will do the project on my own because I am awesome. I will not collaborate with others because I know Hoffman will catch me, (he has code comparison tools) and because I have too much pride for that.

Sign these problems (either electronically or print, sign and take a picture) and turn in an image:
Probs1and2.jpg

HW4 Problem 3 (20pts) Synthesize your UART

Started as Exercise14 on Mon Mar 23rd

- In HW3 you produced a UART transmitter (UART_tx.sv) and a UART receiver (UART_rx.sv). Combine the two module (by simply instantiating each) into a UART transceiver (UART.sv).
- In this HW you will synthesize both modules using Synopsys on the CAE linux machines.
- **NOTE:** We started this as an exercise and you might have done it with a partner. That is fine, but both submit individually.
- Write a synthesis script to synthesize your UART.sv. The script should perform the following:
 - Defines a clock of 500MHz frequency and sources it to clock
 - Performs a set don't touch on the clock network
 - Defines input delays of 0.5 ns on all inputs other than clock
 - Defines a drive strength equivalent to a 2-input nand of size 1 from the Synopsys 32nm library (NAND2X1_RVT) for all inputs except clock and rst_n
 - Defines an output delay of 0.5ns on all outputs.
 - Defines a 0.10pf load on all outputs.
 - Sets a max transition time of 0.15ns on all nodes.
 - Employs the Synopsys 32nm wire load model for a block of size 16000 sq microns
 - Compiles, then flattens the design so it has no hierarchy, and compiles again.
 - Produces a min_delay & max delay report
 - Produces an area report
 - Flattens the design so it has no hierarchy
 - Writes out the gate level verilog netlist (**UART.vg**)
 - Writes out a SDC file. (**UART.sdc**)
- Submit to the dropbox.
 - Your synthesis scripts (UART.dc)
 - The output reports for area (UART_area.txt)
 - The gate level verilog netlist (UART.vg)

HW4 Problem 4 (25pts) UART Wrapper

Started as Exercise 15 on Weds Mar 25th


- The Logic Analyzer receives 16-bit command from the IC. These commands are sent via UART (a byte based protocol). You need to create a wrapper to package two bytes into a single 16-bit command.

- A diagram of the datapath and control needed are shown

- All commands to the Logic analyzer are responded to with at least 1-byte responses. (Either a positive acknowledge, or data read, or a dump of channel data)


- Create **UART_wrapper.sv**.

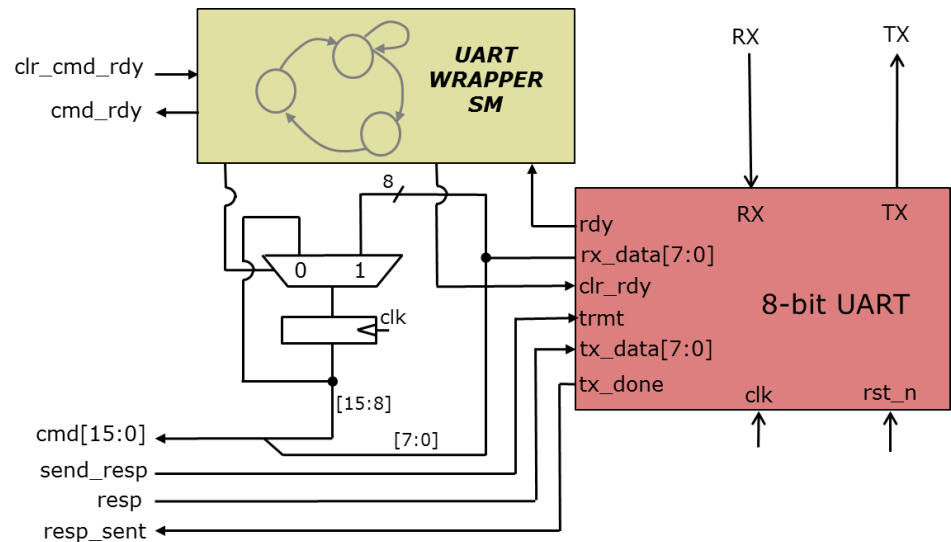- Testing **UART_wrapper** on its own is not so productive. See the next 2 slides first.




HW4 Problem 4 (25pts) CommMaster

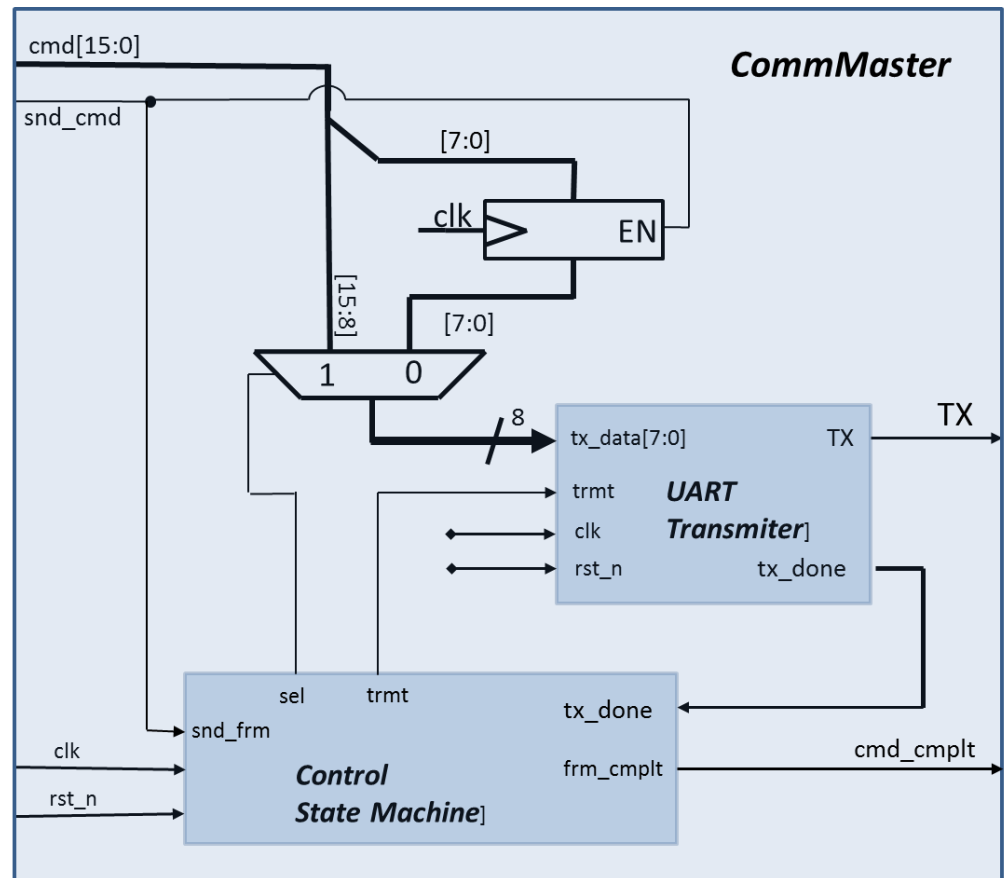- The last problem on your midterm was creating **CommMaster.sv** that did the opposite (took a 16-bit command and sent it as two 8-bit bytes over UART).
- Create **CommMaster.sv**
- See next slide for testing hints.



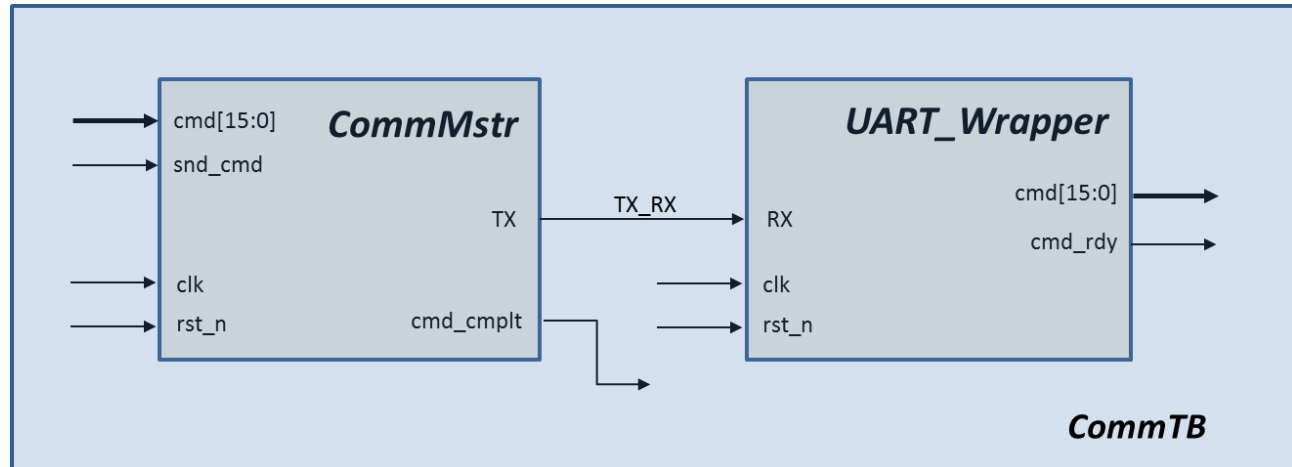HW4 Problem 4 (25pts) Testing UART_wrapper and CommMaster



- Once you have both **CommMstr** and **UART_wrapper** creating a self checking testbench is easier. Simply instantiate both as shown above.
- Send a 16-bit command via **CommMstr**. Look for **cmd_rdy**. When it asserts does the received **cmd** match the sent command?
- Submit **UART_wrapper.sv**, **CommMaster.sv**, and **CommTB.sv** to the dropbox.


HW4 Problem 5 (35pts) SPI receiver for use as protocol

Started as Exercise 16 on Mon Mar 30th


What is SPI

- Simple uni-directional serial interface (Motorola long long ago)
 - Serial Peripheral Interconnect (very popular physical interface)
 - 4-wires for full duplex
 - ✓ MOSI (Master Out Slave In) (digital core will drive this to AFE)
 - ✓ MISO (Master In Slave Out) (not used in connection to AFE digital pots, only EEP)
 - ✓ SCLK (Serial Clock)
 - ✓ SS_n (Active low Slave Select) (Our system has 4 individual slave selects to address the 4 dual potentiometers, and a fifth to address the EEPROM)
 - There are many different variants
 - ✓ MOSI Sampled (shifted) on clock low vs clock high
 - ✓ SCLK normally high vs normally low
 - ✓ Widths of packets can vary from application to applications
 - ✓ Really is a very loose standard (barely a standard at all)
 - We will stick with SCLK normally low, but have configuration for the rest
 - ✓ MOSI sampled on SCLK rise if **edg** is high, SCLK fall if **edg** is low.
 - ✓ 8-bit packets if **len8_16** is high, and 16-bit packets if **len8_16** is low.

SPI Packets

 

 
Shown above is a 16-bit SPI packet where the master is changing (shifting) MOSI on the falling edge of SCLK. This is a case where one would probably choose to have **edg** high so MOSI was sampled on SCLK rise.



Shown above is an 8-bit SPI packet where the master is changing (shifting) MOSI on the rising edge of SCLK. This is a case where one would probably choose to have **edg** low so MOSI was sampled on SCLK fall.

SPI Unit for Protocol Triggering

- Make a SPI_RX module. It should not operate with **SCLK** as a clock, but rather treat **SCLK** as a signal it samples using the main 100MHz system **clk**.
- The SPI module should continue to sample and shift **MOSI** (on the specified edge of **SCLK** (specified by **edg**)) until **SS_n** returns high.
- When **SS_n** returns high the SPI transaction can be considered complete and the contents in the receive shift register can be compared to **match[15:0]**.
- if **len8_16** is high then comparison is only 8-bits, and the lower 8-bits of the receive shift register are compared against **match[7:0]**.
- If **edg** is high then the receive shift register should shift (sample **MOSI**) on the rise of **SCLK**. If **edg** is low then the shift is on the fall of **SCLK**.
- Mask is used to mask off the bits of match and treat them as a don't care in the comparison. High bits in mask represent bits of match that should be treated as don't care.

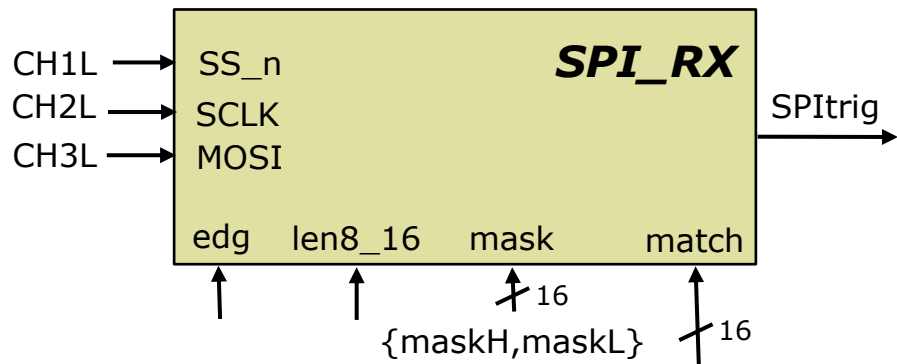

Signal:	Dir:	Description:
clk, rst_n	in	100MHz system clock and reset
SS_n, SCLK, MOSI	in	SPI protocol signals. Coming from VIL comparators
edg	in	When high the receive shift register should shift on SCLK rise.
len8_16	in	When high we are doing an 8-bit comparison to match[7:0]
mask[15:0]	in	Used to mask off bits of match to a don't care for comparison
match[15:0]	in	Data unit is looking to match for a trigger
SPItrig	out	Asserted for 1 clock cycle at end of a reception if received data matches match

HW4 Problem 5 (35pts) SPI receiver for use as protocol trigger

- Create SPI_RX block
- Download SPI_TX module from the HW4 folder that you can use for testing.
- Link the two blocks together to form a self-checking test bench.
- Submit:
 - SPI_RX.sv
 - SPI_tb.sv
 - Output from your self checking test bench proving you ran it successfully